



Dec. 15th, 1928


Modulated R. F. Oscillator Facilitates Receiver Testing

With the possible exception of a voltmeter or ammeter there is no more valuable instrument for the experimenter or service man than a modulated radio-frequency oscillator. Such an oscillator, to-vacuum tube voltmeter described in issue No. 3 of the RADIOBUILDER, and an A.C. voltmeter, comprise the most important elements of a good test outfit.


The unit described below may be constructed from standard parts that should be on the shelf of any S-M service station. It may be built in less than an hour, at very little cost, and the multiplicity of uses to which it may be put make it invaluable.

It may be used as a variable radio-frequency oscillator to cover the broadcast band, as a fixed frequency audio-frequency oscillator working at about 300 cycles, or as a modulated radio-frequency oscillator.

The advantage of using such a unit to determine the general nature of any trouble in a receiver lies in the fact that the test is made under actual operating conditions. Voltage and current readings of direct and power frequency alternating currents do not have to be translated into troubles at radio and audio-frequencies. Once the general nature of the trouble has been determined with the oscillator the other measurements may be used to find the specific cause.

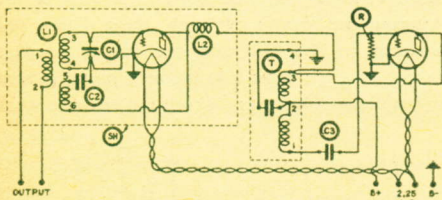

The aluminum shield houses the radio-frequency oscillator circuit, which uses a 227 type tube in a conventional tuned grid oscillator circuit. The coil, condenser, socket and radio-frequency choke are arranged in it as shown in the photograph. The coil socket is mounted on 3/4 inch studs which raise the coil sufficiently to place it symmetrically with respect to the shield. The variable condenser is fastened to the base board with machine screws which are countersunk from the under side. The small fixed condenser immediately to the right of the coil base is the .00025 mfd. condenser shown in the schematic wiring diagram.

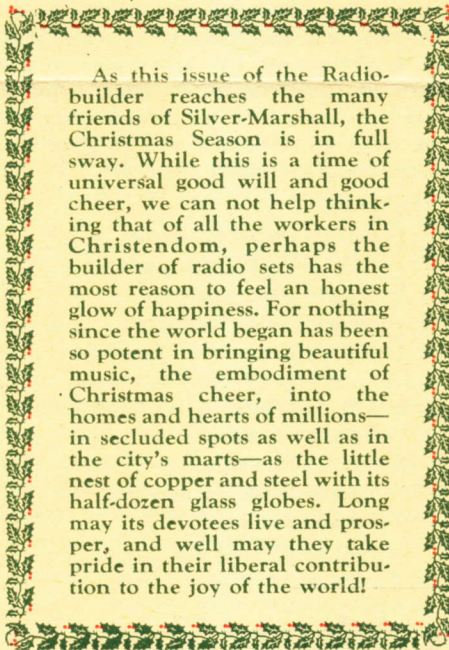

As this issue of the Radiobuilder reaches the many friends of Silver-Marshall, the Christmas Season is in full sway. While this is a time of universal good will and good cheer, we can not help thinking that of all the workers in Christendom, perhaps the builder of radio sets has the most reason to feel an honest glow of happiness. For nothing since the world began has been so potent in bringing beautiful music, the embodiment of Christmas cheer, into the homes and hearts of millions—in secluded spots as well as in the city's marts—as the little nest of copper and steel with its half-dozen glass globes. Long may its devotees live and prosper, and well may they take pride in their liberal contribution to the joy of the world!

The Fahnestock clips, reading from left to right, should be connected to ground and B-, B+, the next two to a 2 to 2.5 volt A.C. source capable of supplying 3.5 amperes, and the right-hand pair are from 1 and 2 of the coil base which in turn connect to the variable coupling coil (rotor). The photograph and schematic wiring diagram show the wiring and assembly clearly.


To use the unit as a straight radio-frequency oscillator, connect a 45 volt B battery to clips 1 and 2, as mentioned above, and a 2.5 volt A.C. source to clips 3 and 4. With a sensitive receiver there will be sufficient coupling to the oscillator if it is placed within a few feet of the receiver. If the receiver gain is low or if the shielding is exceptionally good more coupling may be provided by grounding one lead of the coupling coil and attaching a few feet of wire (to serve as a small antenna) to the other coupling coil clip.

To calibrate the oscillator, tune in some reliable broadcasting station on a receiver and vary the oscillator condenser (with A.F. tube removed) setting until the beat frequency is very low. Using the dial setting of the oscillator and the frequency or wavelength of the station, one calibration point may be plotted on "cross-section" or co-

ordinate paper. Eight or ten such points properly spaced will permit a smooth curve to be drawn. The condenser used gives very nearly a straight-line wave-length curve. This particular coil and condenser gave wave-lengths of 300, 400 and 500 meters at dial settings of approximately 30, 60 and 90 respectively. The unit should be calibrated with the shield in place and it should not be removed when the calibration chart is to be used since the frequency is changed several per cent.

If close coupling to some circuit is wanted, a coil of 8 or 10 turns, 2.5 or 3 inches in diameter, should be connected to clips 5 and 6. This coil is coupled to the external circuit. In using the unit, it was found that sufficient coupling could be used to induce a current of 40 milliamperes in a good circuit without upsetting the frequency of the oscillator more than 0.2 of one per cent.

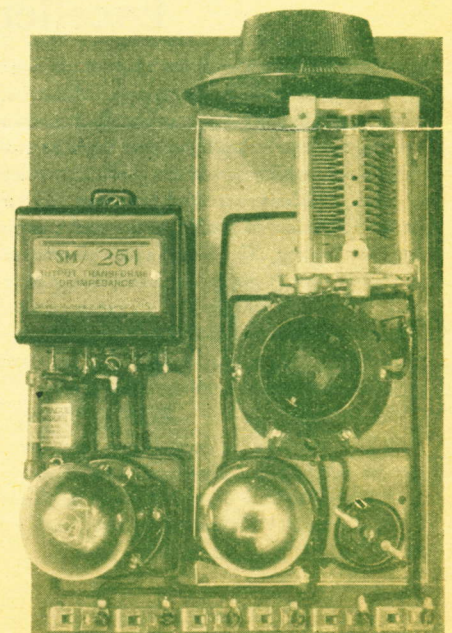Once the unit is calibrated, the reverse procedure may be used to determine the frequency of some broadcast station. If the calibration has been carefully made and if the heater and B battery voltages are kept reasonably constant, and using the same 227 r.f. tube, it will be accurate within a fraction of one per cent. When fishing for



DX the oscillator (with A.F. tube removed) may be made to beat with the DX station and produce

